

VLSI Architectures for Digital Signal Processing

Dr Noor Mahammad Sk

High Performance Reconfigurable Computing System Engineering Group
Indian Institute of Information Technology Design and Manufacturing
(IIITDM) Kancheepuram, Chennai – 600127.



High Performance Circuit Design

◆ High speed Adder Circuits

- Carry Ripple – Inherently Sequential
- Carry Look ahead – Parallel version
- You should understand the conversion portion

◆ Multipliers

- Wallace-tree multipliers


High Performance Circuit Design

- ◆ Performance of a circuit
 - Circuit depth – maximum level in the topological sort.
 - Circuit Size – Number of combinational elements.
- ◆ Optimize both for high performance.
- ◆ Both are inversely proportional – so a balance to be arrived.

Carry Ripple Adder


- ◆ Given two n -bit numbers
 - $(a(n-1), a(n-2), a(n-3), \dots, a(0))$ and
 - $(b(n-1), b(n-2), b(n-3), \dots, b(0))$.
- ◆ A full adder adds three bits (a, b, c), where ' a ' and ' b ' are data inputs and ' c ' is the carry-in bit.
- ◆ It outputs a sum bit ' s ' and a carry-out bit ' co '

Full Adder

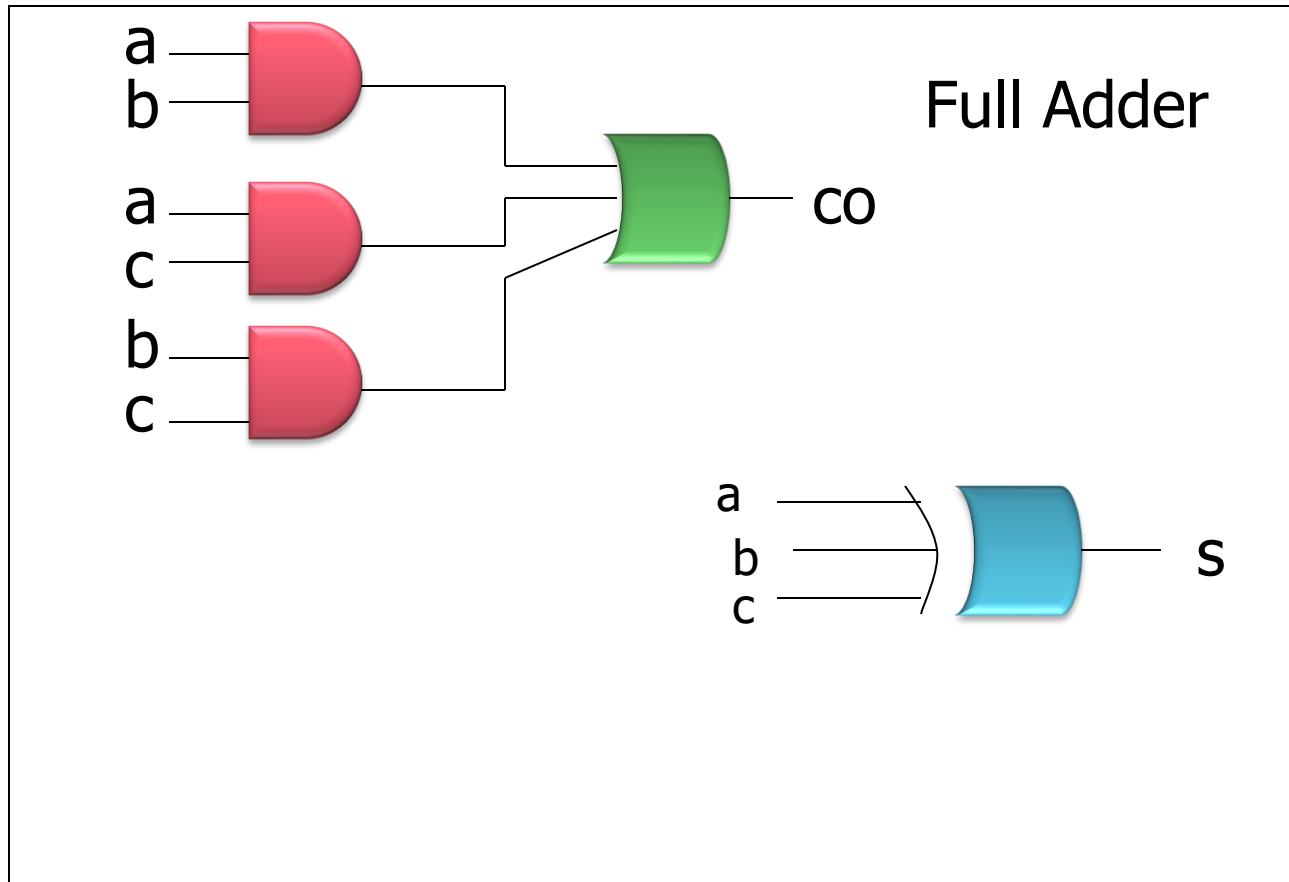

n-bit Carry Ripple Adder

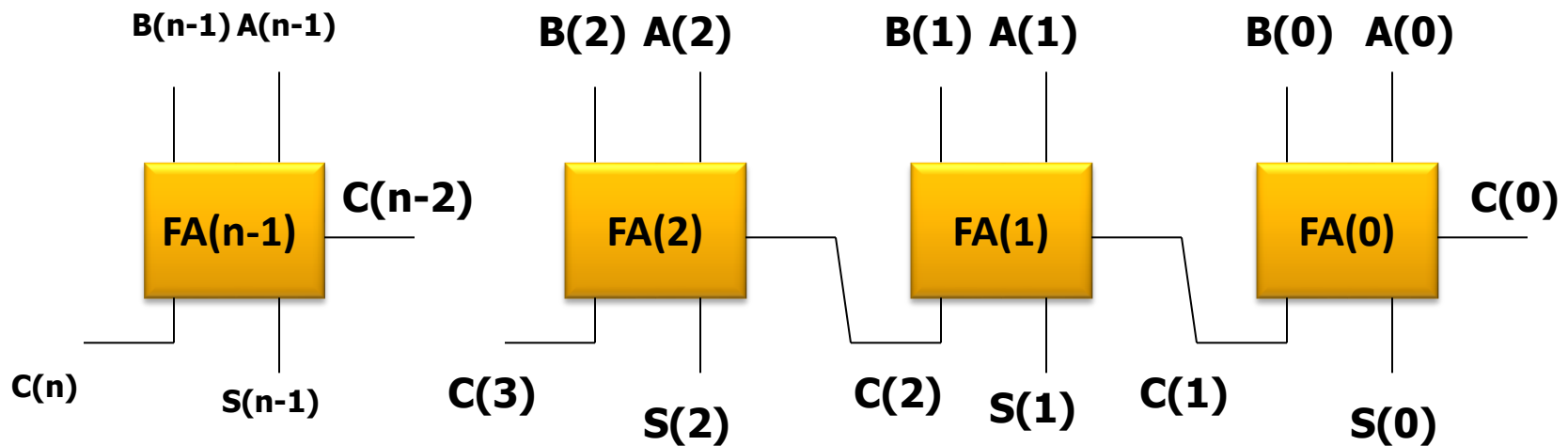- ◆ Circuit Depth is 'n'.
- ◆ Circuit area is 'n' times size of a Full Adder



Carry Lookahead Adder

- ◆ The depth is 'n' because of the carry.
- ◆ Some interesting facts about carry

a(j)	b(j)	c(j)	c(j+1)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

If $a(j) = b(j)$ then

$$c(j+1) = a(j) = b(j)$$

If $a(j) \neq b(j)$ then

$$c(j+1) = c(j)$$

Carry Lookahead Circuit

a(j)	b(j)	c(j)	Status x(j+1)
0	0	0	Kill (k)
0	0	1	
0	1	c(j) = 0	Propagate (p)
0	1	c(j) = 1	
1	0	c(j) = 0	Propagate (p)
1	0	c(j) = 1	
1	1	0	Generate (g)
1	1	1	

Carry Lookahead Circuit

	$x(j+1)$		
$x(j)$	(*)	k	p
	k	k	g
	p	k	p
	g	k	g

← New (j+1)th carry status
as influenced by $x(j)$

(*) is associative

$$y(j) = x(0) (*) x(1) (*) \dots x(j)$$

$$x(0) = k$$

$$\text{If } y(j) = k \text{ then } c(j) = 0$$

$$\text{If } y(j) = g \text{ then } c(j) = 1$$

Note that $y(j) \neq p$

Carry Calculations

◆ A prefix computation

- $y(0) = x(0) = k$
- $y(1) = x(0) (*) x(1)$
- $y(2) = x(0) (*) x(1) (*) x(2)$
-
- $y(n) = x(0) (*) x(1) (*) \dots x(n)$

◆ Let $[i,j] = x(i) (*) x(i+1) (*) \dots x(j)$

◆ $[i,j] (*) [j+1,k] = [i,k]$


- By associative property

Parallel Prefix Circuit

- ◆ Input $x(0), x(1), \dots, x(n)$ – for an n -bit CLA, where $x(0) = k$.
- ◆ Each $x(i)$ is a 2-bit vector
- ◆ To compute the prefix $(*)$ and pipeline the same.
- ◆ $y(i) = x(0) (*) x(1) (*) \dots x(i)$
- ◆ We can use the Recursive Doubling Technique described as follows


An 8-node Carry Lookahead Adder

Parallel Prefix Circuit

 


Parallel Techniques: Recursive Doubling

◆ Finding Prefix sum of '8' numbers

 


Recursive Doubling (Step 1)

◆ Finding Prefix sum of '8' numbers

 


STEP 1

Recursive Doubling (Step 2)

 


STEP 2


Recursive Doubling (Step 3)

 


STEP 3

- 
- ◆ Prefix Sum of n numbers in $\log n$ steps
 - ◆ Recursive Doubling is applicable:
 - Operators like Min, Max, Mul etc. that is associative

 Prefix Calculation Based on Recursive Doubling Technique



 Pipeline Prefix Calculation Based on Recursive Doubling Technique



Outcome of Above Method

- ◆ Depth of the circuit reduced from $O(n)$ to $O(\log_2 n)$
- ◆ Size is still $O(n)$
- ◆ This results in a Fast Adder

Multipliers

- ◆ Simple grade-school multiplication method.
 - Concept of partial-products
- ◆ Partial products generated in parallel and carry save addition results in faster array multiplier

Grade School Multiplication

$$1\ 1\ 1\ 0 = a$$

$$1\ 1\ 0\ 1 = b$$

$$1\ 1\ 1\ 0 = m(0)$$

$$0\ 0\ 0\ 0 = m(1)$$

$$1\ 1\ 1\ 0 = m(2)$$

$$1\ 1\ 1\ 0 = m(3)$$


$$1\ 0\ 1\ 1\ 0\ 1\ 1\ 0 = p$$

Array Multiplier


- ◆ Combination circuit
- ◆ Product generated in one micro-operation
- ◆ Requires large number of gates
- ◆ Became feasible after integrated circuits developed
- ◆ Needed for ' j ' multiplier and ' k ' multiplicand bits
 - $j \times k$ – AND gates
 - $j - 1$ k -bit adders to produce product of $j + k$ bits

2-bit by 2-bit Array Multiplier

		b_1	b_0
	a_1	$a_1 b_1$	$a_1 b_0$
	a_0	$a_0 b_1$	$a_0 b_0$
c_3	c_2	c_1	c_0

 

4-bit by 3-bit array multiplier

 

Carry Save Addition


- ◆ Given three n -bit numbers x , y and z .
- ◆ The circuit computes a n -bit number ' u ' and a $(n+1)$ -bit number ' v ' such that
 - $x+y+z = u + v$

Carry Save Addition Example

8	7	6	5	4	3	2	1	0	i
0	0	0	1	1	1	0	1	1	= x
1	1	0	0	0	0	1	0	1	= y
1	0	0	1	0	1	1	0	0	= z

	0	1	0	0	1	1	1	0	= u
1	0	0	1	0	1	0	1	0	= v

Carry Save Adder Circuit

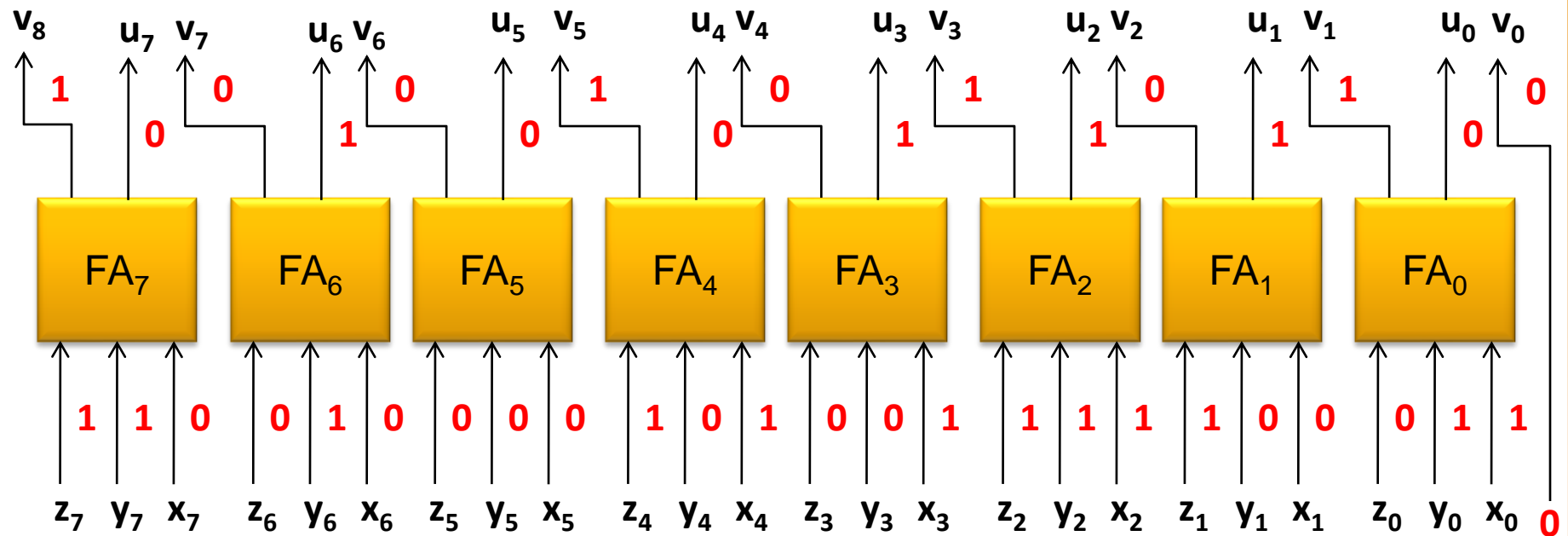


Carry Save Addition based Multiplication

				0	0	0	0	=	0
				1	1	1	0	=	m(0)
			0	0	0	0		=	m(1)
		0	1	1	1	0		=	u(1)
		0	0	0				=	v(1)
	1	1	1	0				=	m(2)
	1	1	0	1	1	0		=	u(2)
	0	1	0					=	v(2)
1	1	1	0					=	m(3)
1	0	1	0	1	1	0		=	u(3)
1	1	0						=	v(3)
1	0	1	1	0	1	1	0	=	p


Wallace Tree Multipliers

- ◆ While multiplying two n -bit numbers a total of n partial products have to be added.
- ◆ Use $\text{floor}(n/3)$ carry save adders and reduce the number to $\text{ceil}(2n/3)$.
- ◆ Apply it recursively.
- ◆ $O(\log n)$ depth circuit of size $O(n^2)$.

8-bit Wallace Tree Multiplication

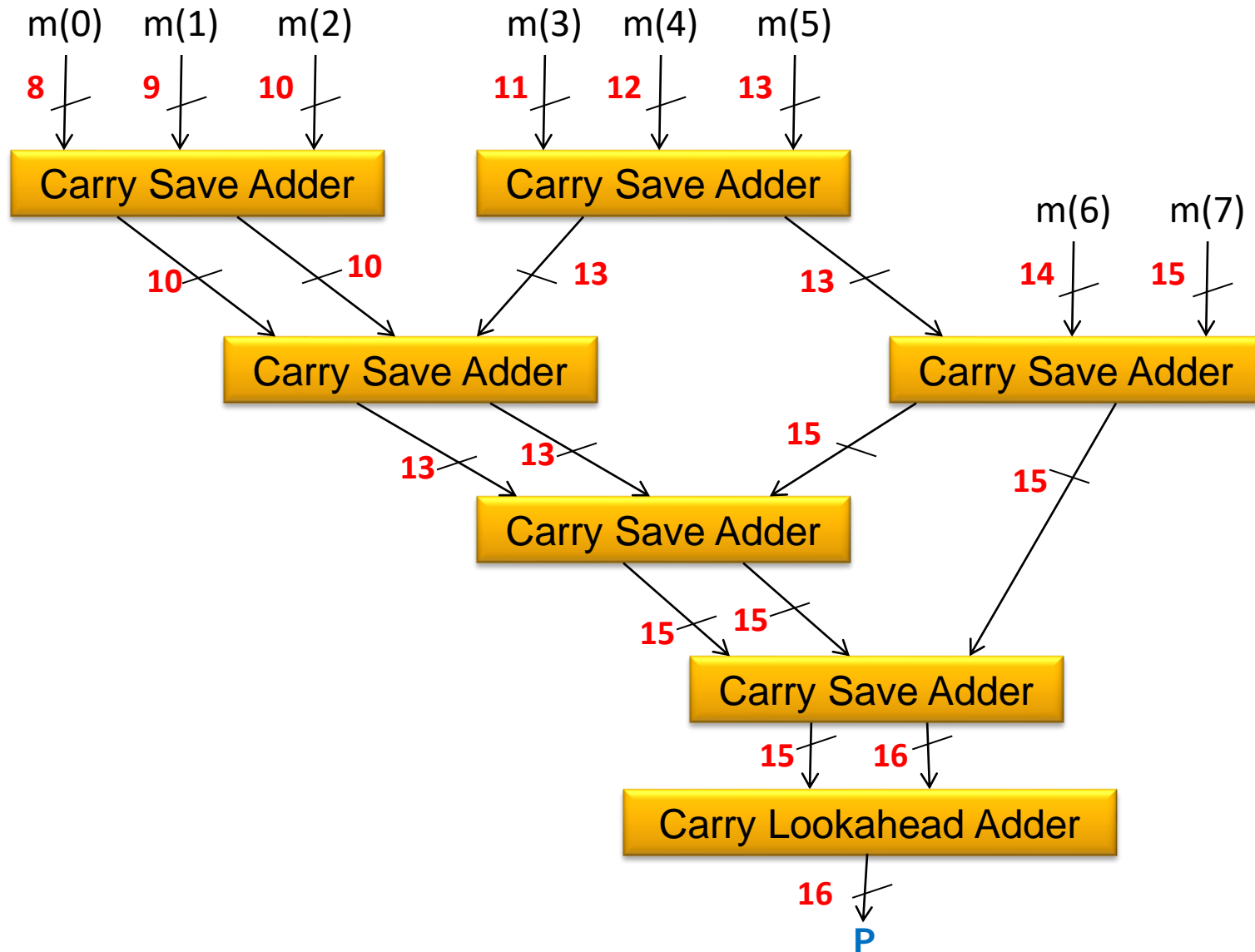

8-bit Wallace Tree Multiplication

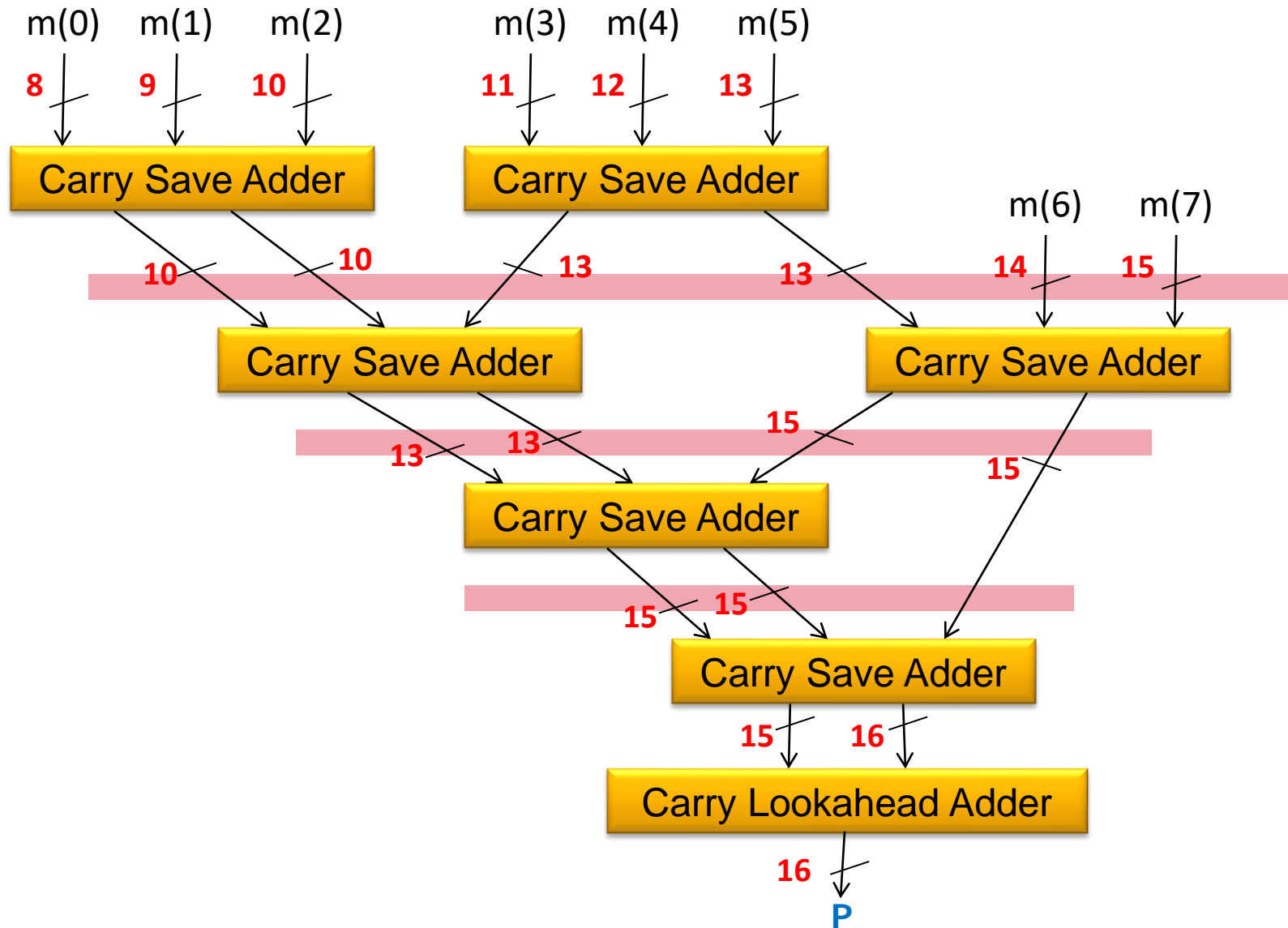

Floating Point Arithmetic



Dr Noor Mahammad Sk

Floating Point Numbers

- ◆ $B = b_0 . b_{-1} b_{-2} \dots b_{-(n-1)}$
- ◆ $F(B) = -b_0 \times 2^0 + b_{-1} \times 2^{-1} + b_{-2} \times 2^{-2} + \dots + b_{-(n-1)} \times 2^{-(n-1)}$
- ◆ IEEE Standards for floating point numbers
 - $\pm X_1 . X_2 X_3 X_4 X_5 X_6 X_7 \times 10^{\pm Y_1 Y_2}$
 - Single Precision (32 – bits)
 - Value represented = $\pm 1. M \times 2^{E' - 127}$ ($E' = E + 127$)
 - Where E stands for Exponent
 - Double Precision (64 – bits)
 - Value represented = $\pm 1. M \times 2^{E' - 1023}$ ($E' = E + 1023$)


Single Precision

◆ Not Normalized

- $0.0010110 \dots \times 2^9$

◆ Normalized

- $1.0110 \dots \times 2^6$

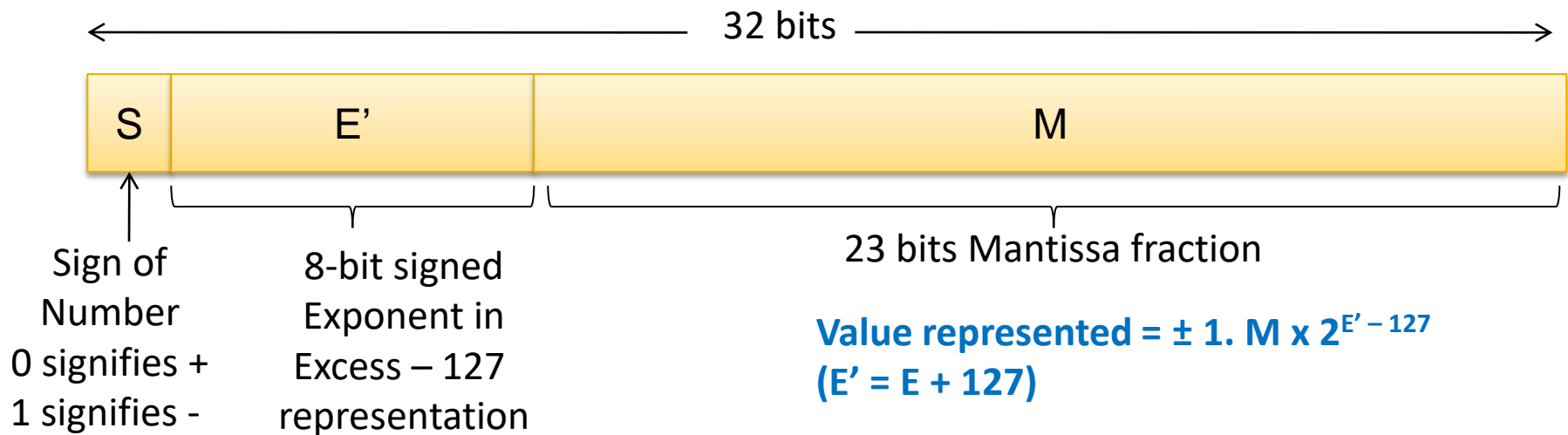


Double Precision

◆ Single Precision

- $1 \leq E' \leq 254$ ($-126 \leq E \leq 127$)

◆ Double Precision

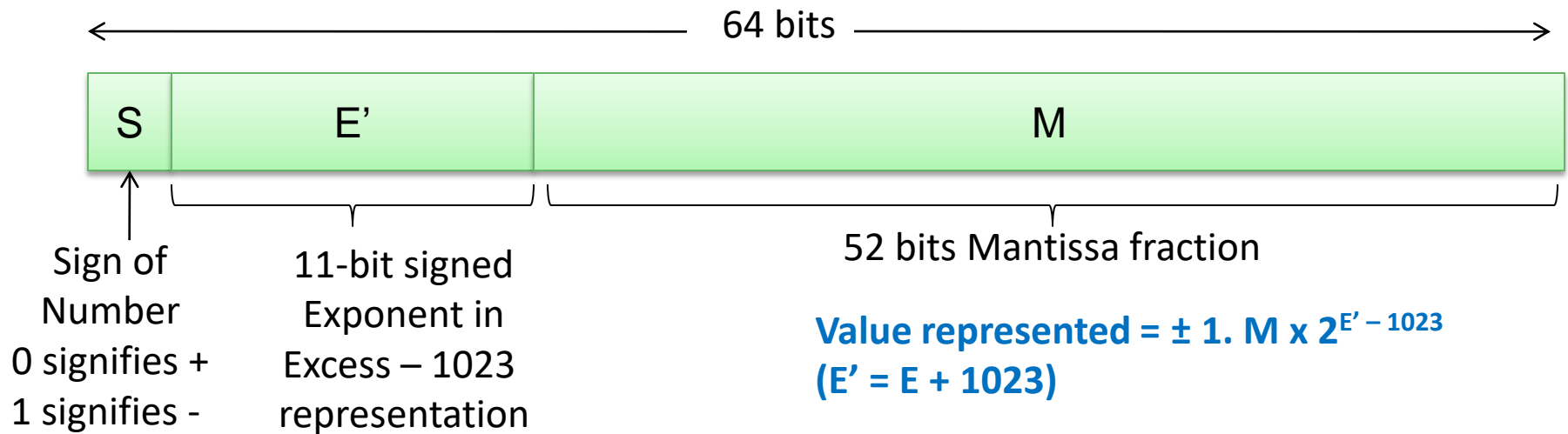- $1 \leq E' \leq 2046$ ($-1022 \leq E \leq 1023$)



Example

0	00101000	001010...	0
---	----------	-----------	---

Value represented = $+ 1.0010110 \dots 0 \times 2^{-87}$

0	10000101	0110 ...
---	----------	----------

Value represented = $+ 1.0110 \dots \times 2^6$

IEEE 754 Format Interpretation

			Single Precision		Double Precision	
	Sign	Fraction	Biased Exponent	Value	Biased Exponent	Value
Positive Zero	0	0	0	0	0	0
Negative Zero	1	0	0	0	0	0
Plus Infinity	0	0	255 (all 1's)	$+\infty$	2047 (all 1's)	$+\infty$
Minus Infinity	1	0	255 (all 1's)	$-\infty$	2047 (all 1's)	$-\infty$
Not a Number	0 or 1	$\neq 0$	255 (all 1's)	NaN	2047 (all 1's)	NaN
Positive normalized nonzero	0	M	$0 < E' < 255$	$2^{E'-127}$ (1.M)	$0 < E' < 2047$	$2^{E'-1023}$ (1.M)
Negative normalized nonzero	1	M	$0 < E' < 255$	$-2^{E'-127}$ (1.M)	$0 < E' < 2047$	$-2^{E'-1023}$ (1.M)
Positive denormalized	0	$M \neq 0$	0	$-2^{E'-127}$ (0.M)	0	$-2^{E'-1023}$ (0.M)
Negative denormalized	1	$M \neq 0$	0	$-2^{E'-127}$ (0.M)	0	$-2^{E'-1023}$ (0.M)

Floating Point Add/ Subtract

- ◆ Check for zeros
- ◆ Align the mantissa
- ◆ Add or subtract mantissas
- ◆ Normalize the result

Multiplication

- ◆ Check for zeros
- ◆ Add the exponents
- ◆ Multiply the mantissas
- ◆ Normalize the product

Floating Point Division

- ◆ Check for zeros
- ◆ Initialize registers and evaluate the sign
- ◆ Align the dividend
- ◆ Subtract the exponents
- ◆ Divide the mantissas

Thank You!!



noor@iiitdm.ac.in