

Laws of Boolean Algebra

Boolean Algebra is an algebraic structure defined by set of elements 'B' together with two binary operators "+" and "."

Operator '+'

1. $x + 0 = x$
2. $x + x' = 1$
3. $x + x = x$
4. $x + 1 = 1$
5. $(x')' = x$
6. $x + y = y + x$
7. $x + (y + z) = (x + y) + z$
8. $x + x.y = x$
9. $(x + y)' = x' . y'$

Operator '.'

- $x . 1 = x$
- $x . x' = 0$
- $x . x = x$
- $x . 0 = 0$
- $x.y = y.x$
- $x . (y . z) = (x.y) . z$
- $x . (x + y) = x$
- $(x . y)' = x' + y'$ (DeMorgans Theorem)

The operator precedence for evaluating Boolean expression is (1) parenthesis (2) NOT (3) AND and (4) OR

Boolean Function


- Boolean algebra deals with binary variables and logic operations.
- A Boolean function described by an algebraic expression consist of binary variables and logic operation symbols and constants 0 and 1.
- For a given value of binary variables, the function can be either 0 or 1.
 - ex. $F = x + y'z$
 F is equals to 1 if $x = 1$ or $y z = 0 1$
- Boolean function expresses logical relationship between binary variables.
- Boolean function can be evaluated by determining the binary value of expression for all possible values of variables
- Boolean function can be transformed from an algebraic expression into circuit diagrams composed of logic gates.

Boolean Function


- There is only one way that a Boolean function can be represented in truth table whereas when the function is in algebraic form, it can be expressed in number of ways having equivalent logic.

- $F = x + y'z$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

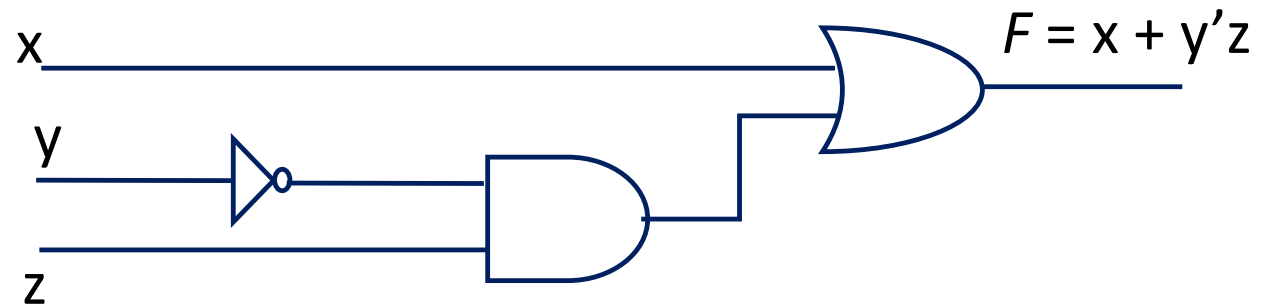


- $F = x + y'z$
 $= (x + y')(x + z)$

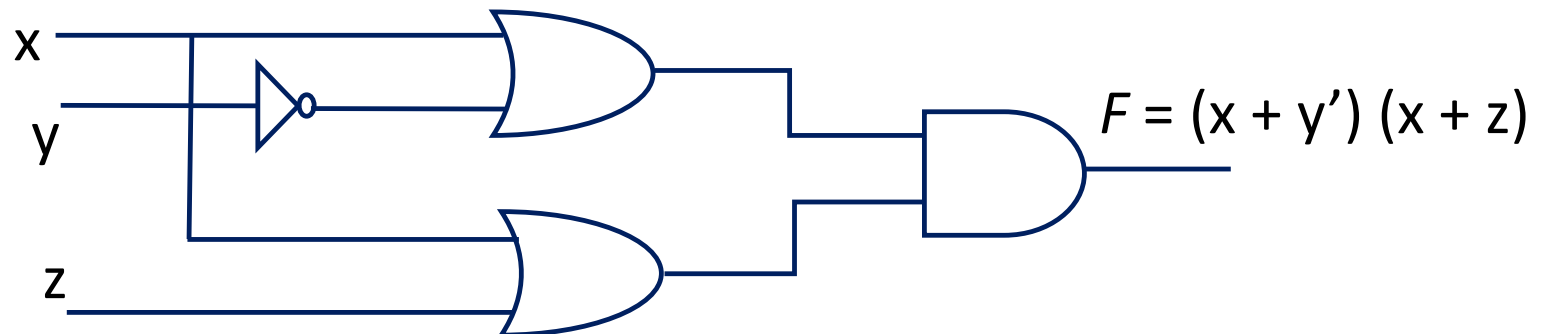

Boolean Function

- By manipulating Boolean expression according to rules of Boolean algebra; it is possible to obtain a simpler expression for the same function, thus reduce number of gates in circuit and number of inputs to the gate.


- Ex. $F_1 = x'y'z + x'yz + xy'$

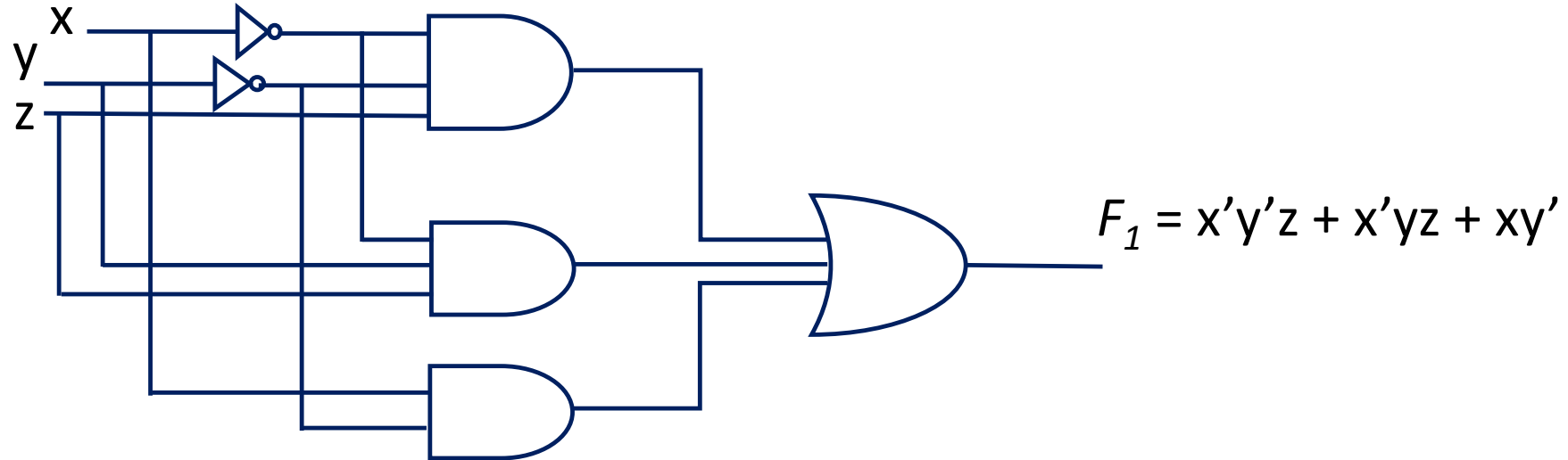

- $F_2 = x'y'z + x'yz + xy'$

$$= x'z(y' + y) + xy'$$

$$= x'z + xy'$$

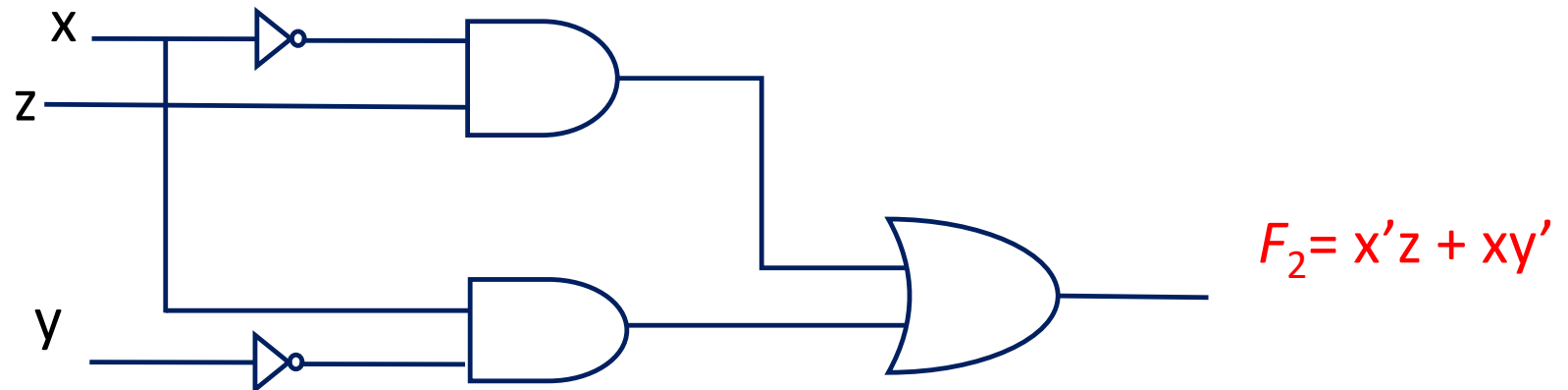

Complement of Function

- Complement of function F is F' and can be derived algebraically by DeMorgans theorem.
- $(A + B + C)' = A'B'C'$
- The generalized DeMorgans's Theorem: Complement of function is obtained by interchanging AND and OR operator and complementing each literal.

ex. Find the complement of Function $F = x'yz' + x'y'z$

$$F' = (x'yz' + x'y'z)'$$

$$F' = (x'yz')' (x'y'z)'$$

$$F' = (x + y' + z) (x + y + z')$$

Canonical forms

Minterms and Maxterms

- Binary variables may appear in normal (x) or complement forms (x').
- For two variables x and y combined with AND operator, there are four possible combinations i.e. $x'y'$, $x'y$, xy' , xy .
- Each of these four AND-terms is called a *minterm* or *standard product*.
- n variables can be combined to form 2^n minterms.
- Each minterm is obtained from an AND-term of n variables, with each variable being *primed* if the corresponding bit of binary number is **0** and unprimed if it is **1**.
- Similarly, n variables forming an OR term, with each variable being primed or unprimed, provide 2^n possible combinations called *maxterms* or *standard sum*.
- Each maxterm is obtained from an OR term of n variables, with each variable being *primed* if the corresponding bit of binary number is **1** and unprimed if it is **0**. ex. $(x+y, x+y', x'+y, x'+y')$
- *Each maxterm is complement of its minterm and vice versa.*

Canonical forms

Minterms and Maxterms for three binary variables

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_4	$x'+y+z'$	M_4
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

Sum of Minterms

- Boolean function can be expressed algebraically, from given truth table by forming minterms of each combination of variable that produces 1 in the function and then taking OR of all the terms (*sum of minterms*).

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Function F_1 can be determine by expressing combinations 001, 100, and 111 as $x'y'z$, $xy'z'$ and xyz respectively, since each one of these minterms result in $F_1 = 1$.
- $F_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$
- Similarly, $F_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7$
- Any Boolean function can be expressed as sum of minterms.*
- Complement of Function can be obtained by forming minterm of each combination that produces **0** in the function and then ORing them.
- Complement of Function F_1 is $F_1' = x'y'z' + x'yz' + x'yz + xy'z + xyz'$

Product of Maxterms

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Complement of Function F_1' is F_1 .
- $F_1 = (x + y + z) (x + y' + z) (x + y' + z') (x' + y + z') (x' + y' + z)$
- $F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$
- *Any Boolean function can be expressed as product of maxterms.*
- Boolean function can be expressed algebraically, from given truth table by forming maxterms of each combination of variable that produces 0 in the function and then taking AND of all the terms (*Product of maxterms*)
- *Boolean functions expressed as sum of minterms or product of maxterms are called canonical form.*

Sum of minterms

- Function which is not in sum of minterms form can be made so by
 - first expanding expression into AND-terms.
 - Each term is inspected to see if it contains all the variables.
 - Missing variables are AND ed with an expression $(x + x')$, where x is missing variable.

Ex. Express function $F = A + B'C$ as sum of minterms.

There are two terms and three variables in the function F .

First term A is missing two variables

$$A = A(B + B')$$

$$= AB + AB'$$

$$= AB(C + C') + AB'(C + C')$$

$$= ABC + ABC' + AB'C + AB'C'$$

Second term $B'C$ is missing one variable

$$B'C = B'C(A + A') = AB'C + A'B'C$$

$$F = ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

$$F = ABC + ABC' + AB'C + AB'C' + A'B'C$$

$$F = m_7 + m_6 + m_5 + m_4 + m_1$$

$$F(A, B, C) = \sum (1, 4, 5, 6, 7)$$

Product of Maxterms

To express Boolean function as a product of maxterm

- Bring the expression in the form of OR terms by distributive law i.e. $x+yz = (x+y)(x+z)$
- Any missing term is then OR ed with $x.x'$, where x is missing variable.

Ex. Express Boolean Function $F = xy + x'z$ as product of maxterms

$$F = xy + x'z$$

$$F = (xy + x')(xy + z)$$

$$(y + x') = (y + x' + zz') = (x' + y + z)(x' + y + z')$$

$$F = (x + x')(y + x')(x + z)(y + z)$$

$$(x + z) = (x + z + yy') = (x + y + z)(x + y' + z)$$

$$F = (y + x')(x + z)(y + z)$$

$$(y + z) = (y + z + xx') = (x + y + z)(x' + y + z)$$

$$F = (x' + y + z)(x' + y + z')(x + y + z)(x + y' + z)(x + y + z)(x' + y + z)$$

$$F = (x' + y + z)(x' + y + z')(x + y + z)(x + y' + z)(x' + y + z)$$

$$= M_0. M_2. M_4. M_5$$

$$F(x, y, z) = \Pi(0, 2, 4, 5)$$

Standard form

- Canonical forms of Boolean algebra are very seldom with least number of literal because each minterms and maxterms must contain all the variables.
- Standard form is another way to express Boolean function.
- Terms of that forms the function may contain any number of literals.
- Two types of Standard forms: **Sum of products and Product of Sum**
- **Sum of product is Boolean expression containing AND-terms, with one or more literals each.**

$$F_1 = y' + xy + x'yz'$$

- **Product of sum : Boolean expression containing OR-terms called sum terms**

$$F_1 = x(y' + z)(x' + y + z')$$