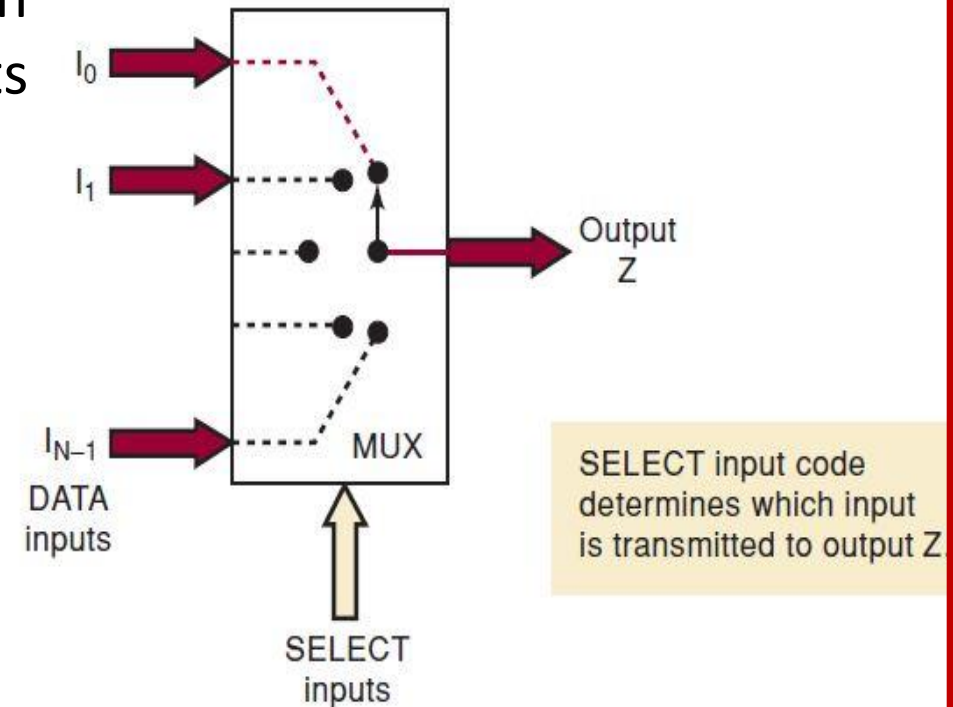


# MULTIPLEXERS (DATA SELECTORS)

- A *digital multiplexer* or *data selector* is a logic circuit that accepts several digital data inputs and selects one of them at any given time to pass on to output.
- Routing of desired data input to output is controlled by SELECT inputs (ADDRESS inputs).
- Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.
- Multiplexer acts as a digitally controlled multi-position switch, where digital code applied to SELECT inputs controls data inputs to be switched to output.
- Output  $Z$  will equal data input  $I_0$  for some particular SELECT input code,  $Z$  will equal  $I_1$  for another particular SELECT input code, and so on.
- Multiplexer selects 1 out of  $N$  input data sources and transmits selected data to a single output channel called **multiplexing**.



## Basic Two- to One line Multiplexer

- Logic level applied to  $S$  input determines which AND gate is enabled so that its data input passes through OR gate to output  $Z$ .

- Boolean expression for output is

$$Z = I_0 S + I_1 \bar{S}$$

- With  $S = 0$

$$Z = I_0 \cdot 1 + I_1 \cdot 0$$

$$= I_0 \quad \text{[gate 2 enabled]}$$


- $Z$  will be identical to input signal  $I_0$ .

- With  $S = 1$


$$Z = I_1 \quad \text{[gate 1 enabled]}$$

- Output  $Z$  will be identical to input signal  $I_1$ .

 - Multiplexer acts like an electronic switch that selects one of two sources.




 *Logic circuit for two-input multiplexer with data inputs  $I_0$  and  $I_1$  and SELECT input  $S$ .*



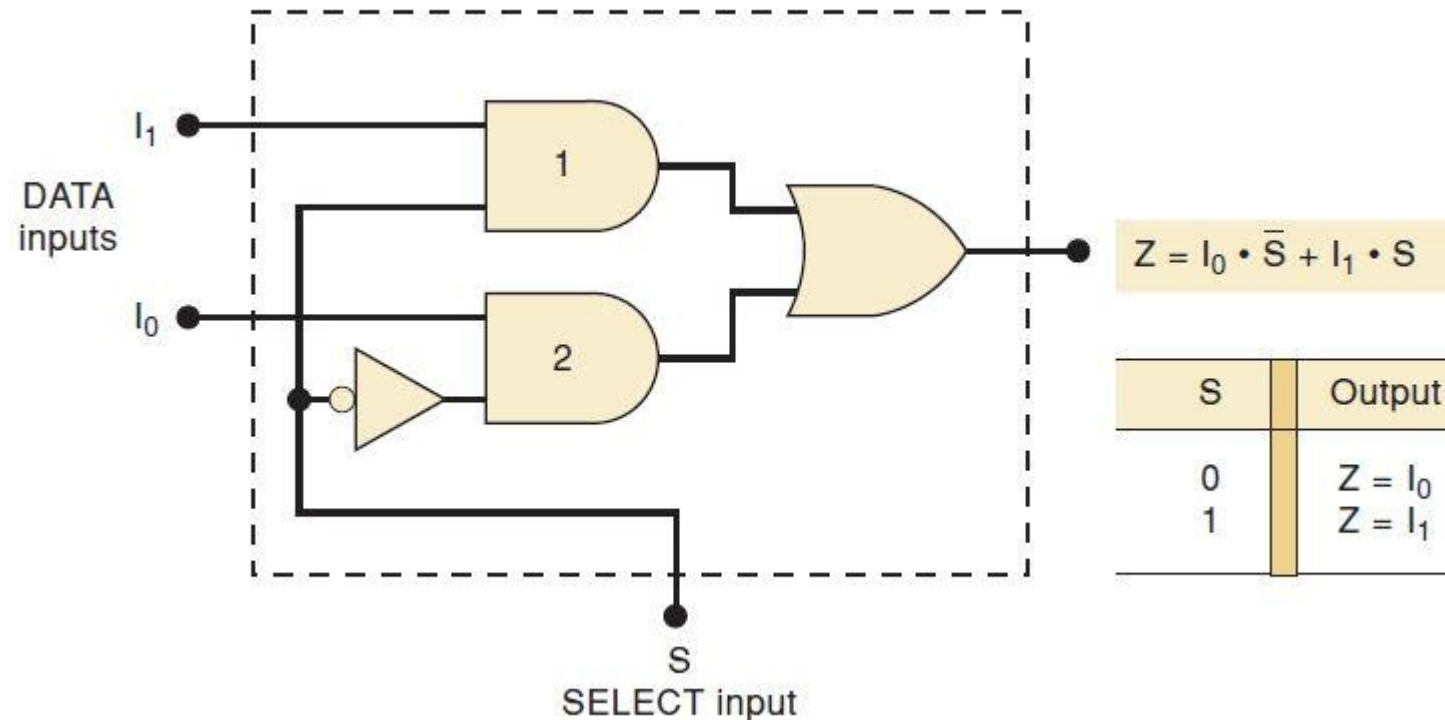
## Basic *Two- to One* line Multiplexer

- Ex. a digital system that uses two different MASTER CLOCK signals: a high-speed clock (say, 10 MHz) in one mode and a slow-speed clock (say, 4.77 MHz) for the other.
- 10-MHz clock would be tied to  $I_0$  and 4.77-MHz clock would be tied to  $I_1$ .
- A signal from the system's control logic section would drive SELECT input to control which clock signal appears at output Z for routing to other parts of the circuit.


 
## Four-to One line Multiplexer

- Each of four inputs,  $I_0$  through  $I_3$ , is applied to one input of AND gate.
- Selection lines  $S_1$  and  $S_0$  are decoded to select a particular AND gate.
- Outputs of AND gates are applied to single OR gate that provides one-line output.
- Consider when  $S_1S_0 = 10$ .
- AND gate associated with input  $I_2$  has two of its inputs equal to 1 and third input connected to  $I_2$ .
- Other three AND gates have at least one input equal to 0, which makes their outputs equal to 0.
- Output of OR gate is now equal to value of  $I_2$ , providing a path from selected input to output.



$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


## ***Four-to One line Multiplexer***

- AND gates and inverters in multiplexer resemble a decoder circuit, and indeed, they decode selection input lines.
- $2^n$  -to-1-line multiplexer is constructed from an  $n$  -to- $2^n$  decoder by adding  $2^n$  input lines to it, one to each AND gate.
- Outputs of AND gates are applied to a single OR gate.
- Size of a multiplexer is specified by number  $2^n$  of its data input lines and single output line.
- $n$ - selection lines are implied from  $2^n$  data lines.
- As in decoders, multiplexers may have an enable input to control operation of the unit.
- When enable input is in inactive state, outputs are disabled, and when it is in the active state, circuit functions as a normal multiplexer.

## Eight- to one line Multiplexer


- This multiplexer has an enable input  $E'$  and provides both normal and inverted outputs.
- When  $E' = 0$ , select inputs  $S_2S_1S_0$  will select one data input (from  $I_0$  through  $I_7$ ) for passage to output  $Z$ .
- When  $E' = 1$ , multiplexer is disabled so that  $Z = 0$ , regardless of select input code.

Inputs				Outputs	
$\bar{E}$	$S_2$	$S_1$	$S_0$	$\bar{Z}$	$Z$
H	X	X	X	H	L
L	L	L	L	$\bar{I}_0$	$I_0$
L	L	L	H	$\bar{I}_1$	$I_1$
L	L	H	L	$\bar{I}_2$	$I_2$
L	L	H	H	$\bar{I}_3$	$I_3$
L	H	L	L	$\bar{I}_4$	$I_4$
L	H	L	H	$\bar{I}_5$	$I_5$
L	H	H	L	$\bar{I}_6$	$I_6$
L	H	H	H	$\bar{I}_7$	$I_7$

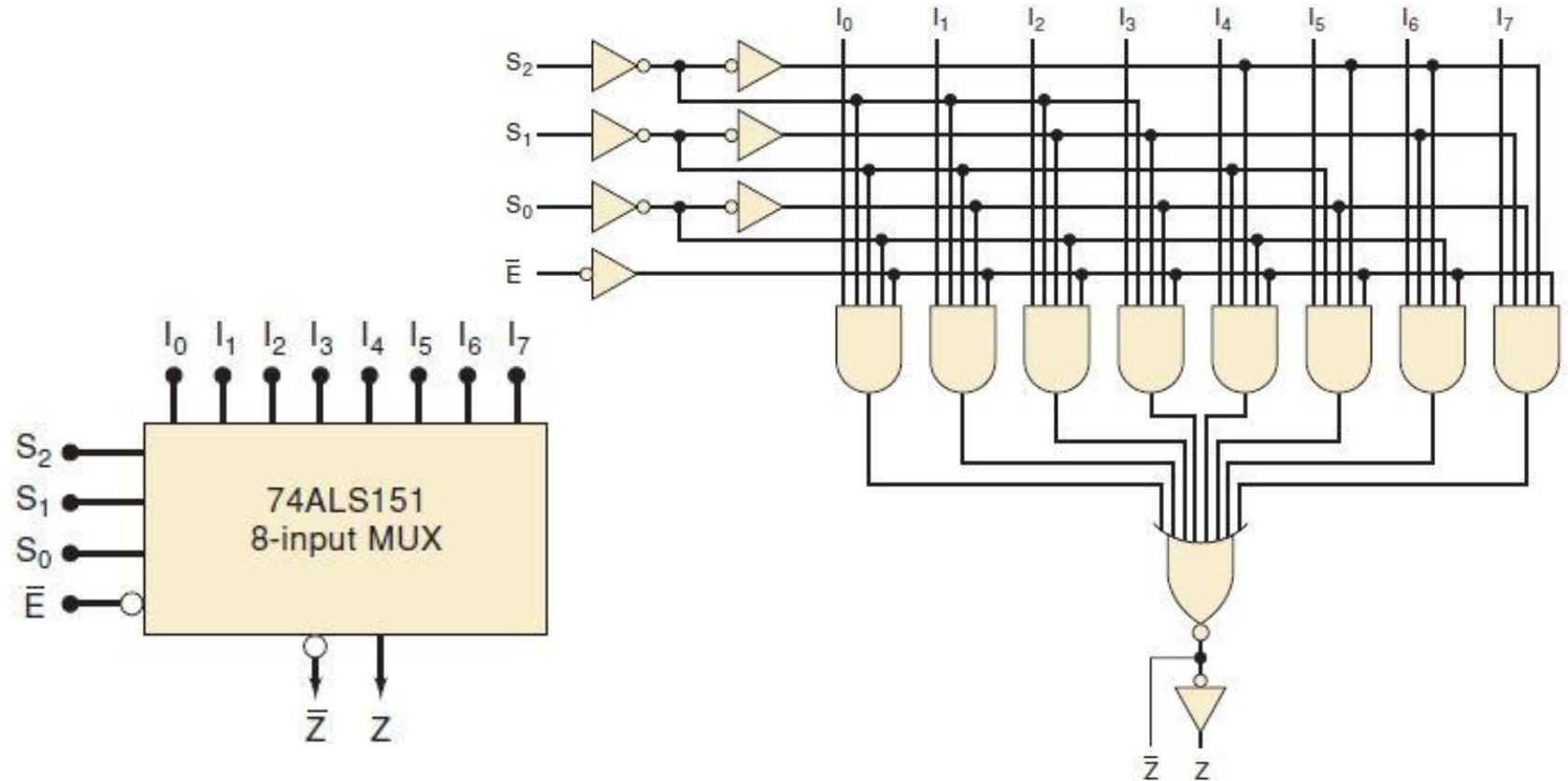
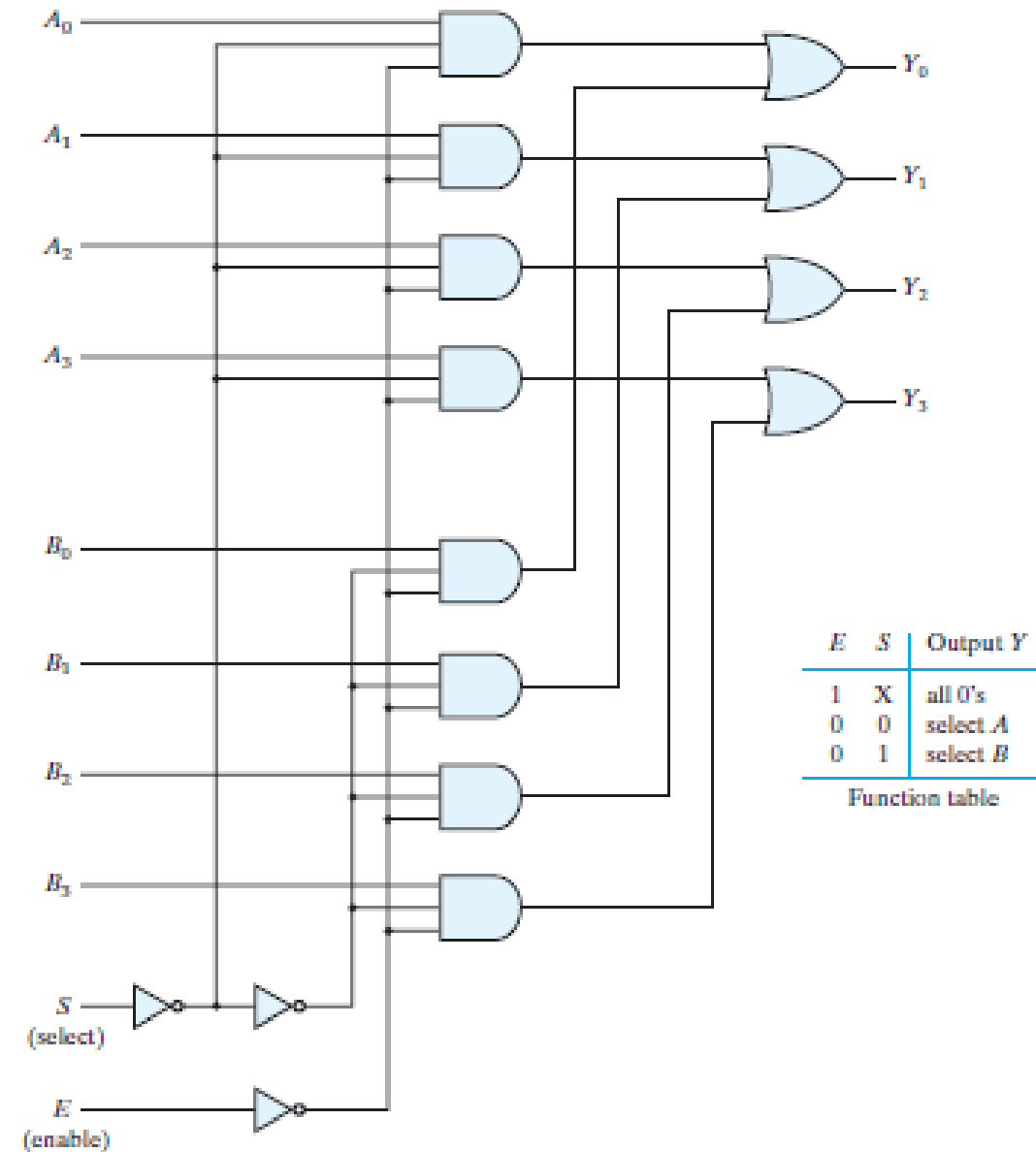
## Quadruple *Two-to-one-line* multiplexer


- Multiplexer circuits can be combined with common selection inputs to provide multiple-bit selection logic.
- The circuit has four multiplexers, each capable of selecting one of two input lines.
- Output  $Y_0$  can be selected to come from either input  $A_0$  or input  $B_0$ .
- Similarly, output  $Y_1$  may have the value of  $A_1$  or  $B_1$ , and so on.
- Input selection line  $S$  selects one of the lines in each of the four multiplexers.
- Enable input  $E$  must be active for normal operation.
- Although circuit contains four 2-to-1-line multiplexers, it is viewed as a circuit that selects one of two 4-bit sets of data lines.




 
# DEMULTIPLEXERS (DATA DISTRIBUTORS)

- A multiplexer takes several inputs and transmits *one* of them to the output.
- A **demultiplexer (DEMUX)** performs reverse operation: it takes a single input and distributes it over several outputs.
- Large arrows for inputs and outputs represent one or more lines.
- The select input code determines to which output DATA input will be transmitted.
- Demultiplexer takes one input data source and selectively distributes it to 1 of  $N$  output channels.






# 1-Line-to-8-Line Demultiplexer

- A demultiplexer that distributes one input line to eight output lines.
- Single data input line  $I$  is connected to all eight AND gates, but only one of these gates will be enabled by the SELECT input lines.
- EX. With  $S_2S_1S_0 = 000$ , only AND gate 0 will be enabled and data input  $I$  will appear at output  $O_0$ .
- Other SELECT codes cause input  $I$  to reach other outputs.


SELECT code			OUTPUTS							
$S_2$	$S_1$	$S_0$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	0	$I$
0	0	1	0	0	0	0	0	0	$I$	0
0	1	0	0	0	0	0	0	$I$	0	0
0	1	1	0	0	0	0	$I$	0	0	0
1	0	0	0	0	0	$I$	0	0	0	0
1	0	1	0	0	$I$	0	0	0	0	0
1	1	0	0	$I$	0	0	0	0	0	0
1	1	1	$I$	0	0	0	0	0	0	0

Note:  $I$  is the data input

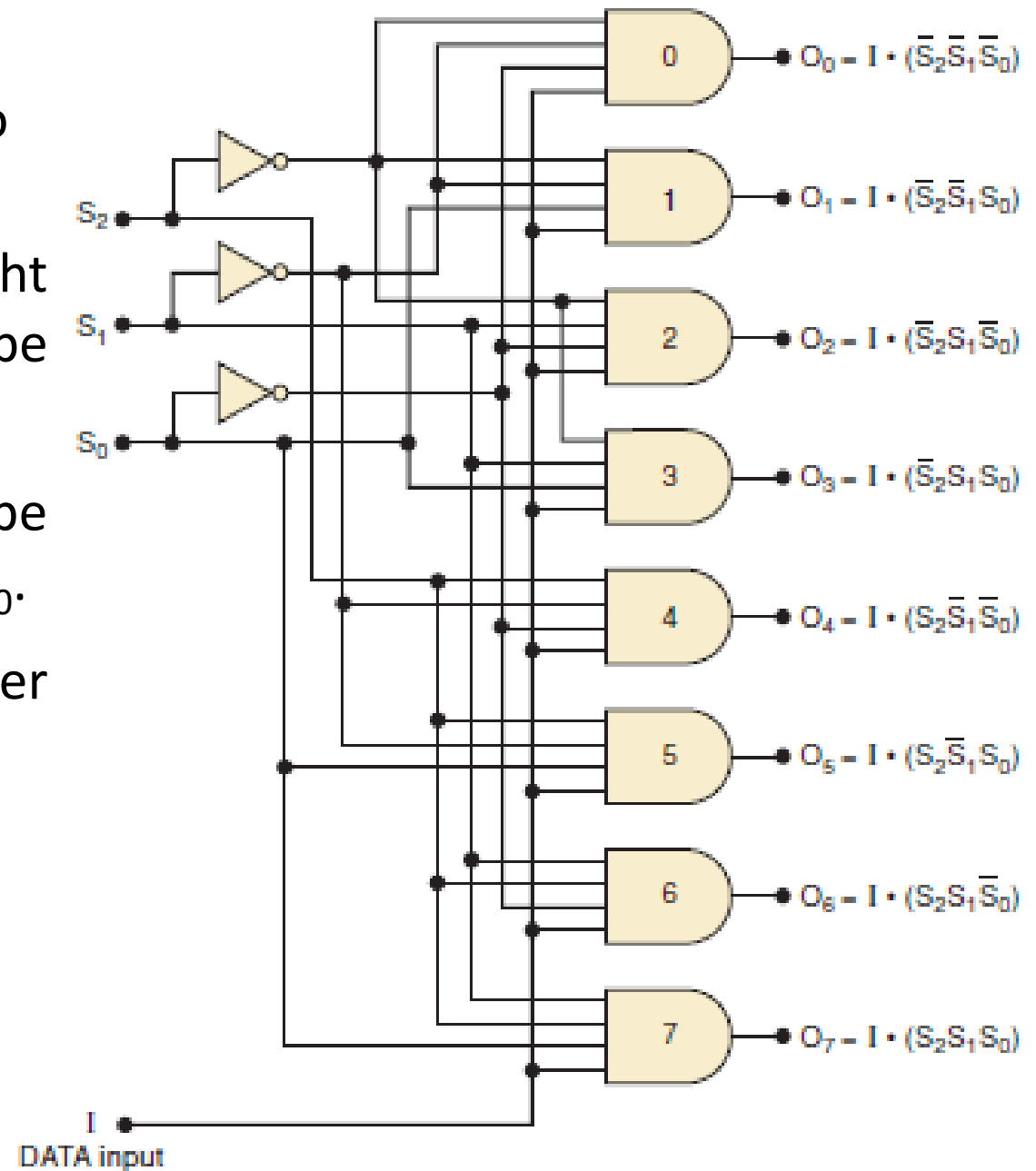

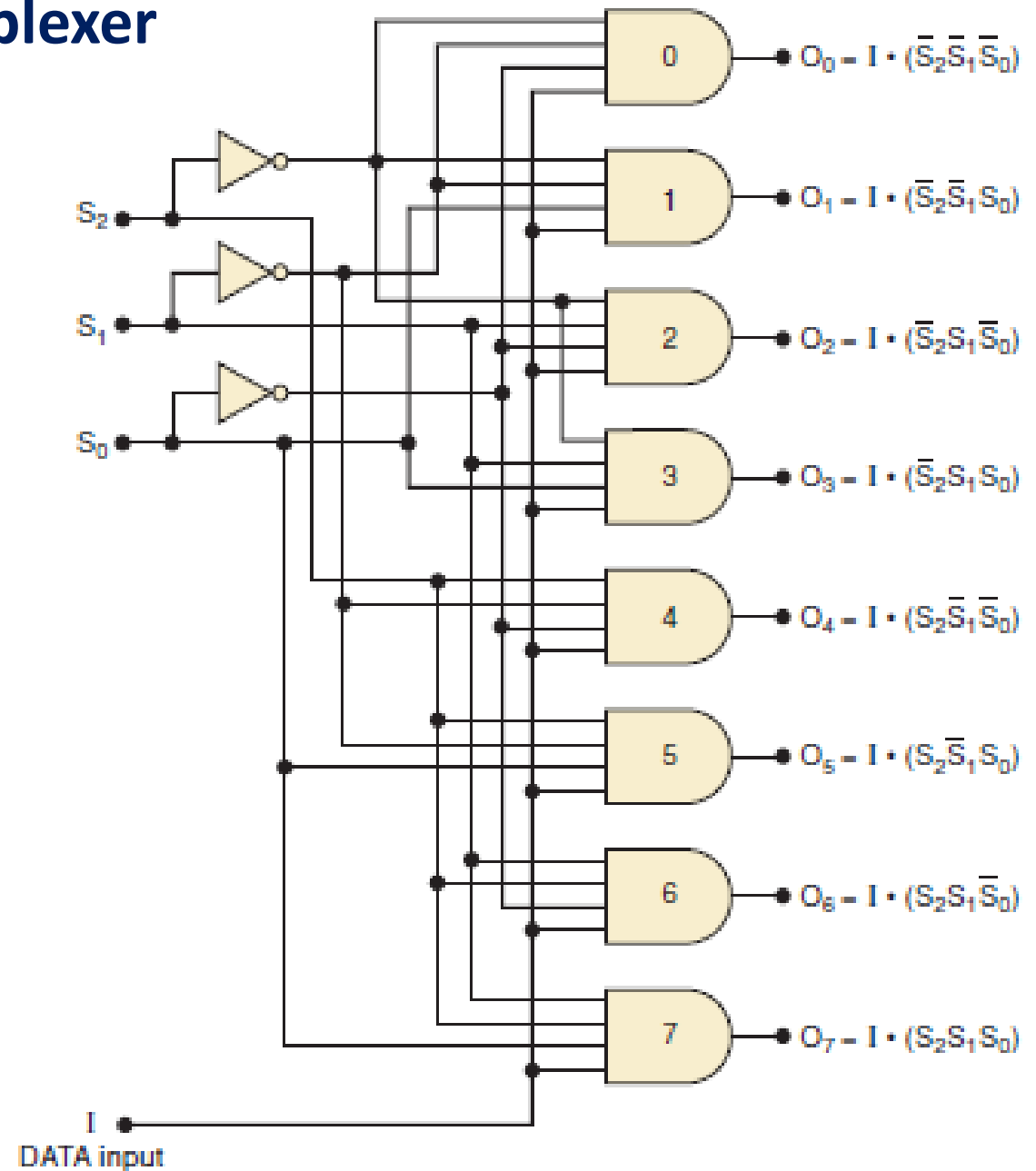
# 1-Line-to-8-Line Demultiplexer

- Demultiplexer circuit is similar to 3-to-8-line decoder circuit except that a fourth input ( $I$ ) has been added to each gate.
- Many IC decoders have an ENABLE input, which is an extra input added to decoder gates.
- This type of decoder chip can therefore be used as a demultiplexer, with the binary code inputs serving as SELECT inputs and ENABLE input serving as the data input  $I$ .
- For this reason, IC manufacturers often call this type of device a *decoder/demultiplexer*, and it can be used for either function.


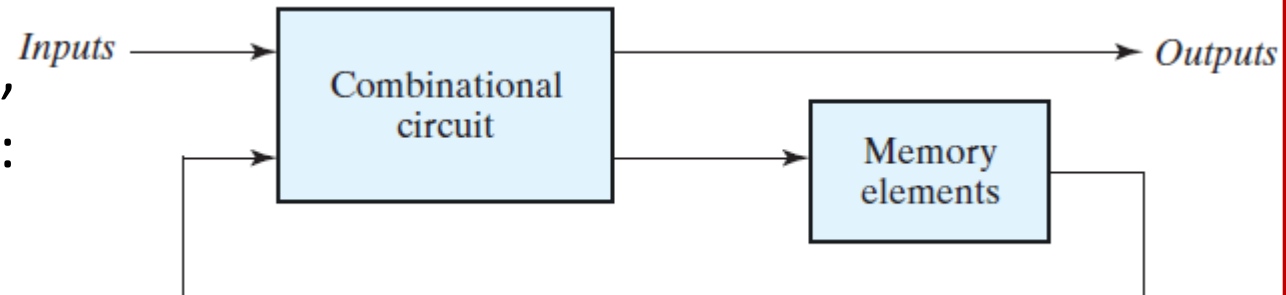
# SEQUENTIAL CIRCUITS

- Sequential circuit receives binary information from external inputs that, together with present state of storage elements, determine binary value of outputs.
- External inputs also determine the condition for changing the state in storage elements.
- Outputs in a sequential circuit are a function not only of the inputs, but also of the present state of the storage elements.
- Next state of the storage elements is also a function of external inputs and present state.
- *A sequential circuit is specified by a time sequence of inputs, outputs, and internal states .*
- In contrast, outputs of combinational logic depend only on the present values of the inputs.
- Two main types of sequential circuits, function of timing of their signals: *synchronous* and *asynchronous*



# SEQUENTIAL CIRCUITS

- **A synchronous sequential circuit:** A system whose behaviour can be defined from knowledge of its signals at discrete instants of time.
- **An asynchronous sequential circuit:** A system whose behaviour depends upon input signals at any instant of time and order in which the inputs change.
- Storage elements used in asynchronous sequential circuits are time-delay devices.
- Storage capability of time-delay device varies with time it takes for signal to propagate through device.
- Internal propagation delay of logic gates is sufficient to produce needed delay, so that actual delay units may not be necessary.
- In gate-type asynchronous systems, storage elements consist of logic gates whose propagation delay provides required storage.
- An asynchronous sequential circuit is a combinational circuit with feedback.
- Because of feedback among logic gates, an asynchronous sequential circuit may become unstable at times hence difficult to design.

# SEQUENTIAL CIRCUITS


- A synchronous sequential circuit employs signals that affect the storage elements at only discrete instants of time.
- Synchronization is achieved by a timing device called a clock generator, which provides a clock signal having form of a periodic train of clock pulses, denoted by **identifiers clock and clk**.
- Clock pulses are distributed throughout system in such a way that storage elements are affected only with arrival of each pulse.
- Clock pulses determine **when** computational activity will occur within the circuit, and other signals (external inputs and otherwise) determine **what** changes will take place affecting the storage elements and the outputs.
- For example, a circuit that is to add and store two binary numbers would compute their sum from the values of the numbers and store the sum at the occurrence of a clock pulse.

# SEQUENTIAL CIRCUITS

- Synchronous sequential circuits that use clock pulses to control storage elements are called *clocked sequential circuits* and are most frequently used.
- They are called synchronous circuits because the activity within the circuit and the resulting updating of stored values is synchronized to the occurrence of clock pulses.
- Design of synchronous circuits is feasible because they seldom manifest instability problems and their timing is easily broken down into independent discrete steps, each of which can be considered separately.
- Storage elements (memory) used in clocked sequential circuits are called *flipflops*.
- A flip-flop is a binary storage device capable of storing one bit of information.
- In a stable state, output of a flip-flop is either 0 or 1.
- A sequential circuit may use many flip-flops to store as many bits as necessary.
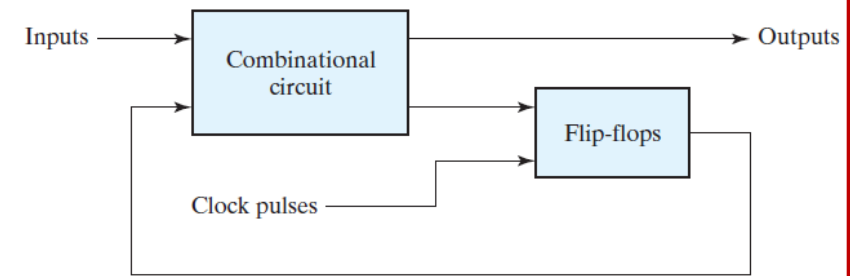
## SYNCHRONOUS CLOCKED SEQUENTIAL CIRCUIT

- Outputs are formed by a combinational logic function of inputs to circuit or values stored in flip-flops (or both).
- Value that is stored in a flip-flop when clock pulse occurs is also determined by inputs to circuit or values presently stored in flip-flop (or both).
- New value is stored (i.e., flip-flop is updated) when a pulse of clock signal occurs
- Prior to the occurrence of clock pulse, combinational logic forming the next value of flip-flop must have reached a stable value.
- Speed at which combinational logic circuits operate is critical.
- If clock (synchronizing) pulses arrive at a regular interval, combinational logic must respond to a change in state of flip-flop in time to be updated before the next pulse arrives.
- Propagation delays play an important role in determining minimum interval between clock pulses that will allow the circuit to operate correctly.



(a) Block diagram




(b) Timing diagram of clock pulses



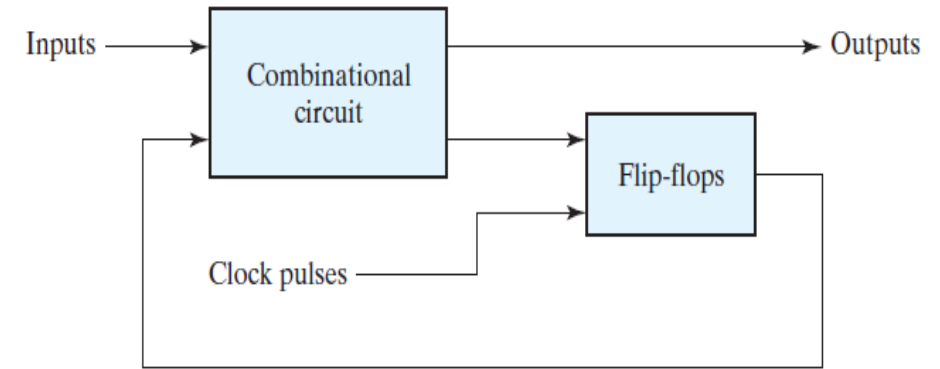
# SYNCHRONOUS CLOCKED SEQUENTIAL CIRCUIT

- A change in state of flip-flops is initiated only by a clock pulse transition—for example, when value of clock signals changes from 0 to 1.
- When a clock pulse is not active, feedback loop between the value stored in the flip-flop and value formed at input to the flip-flop is effectively broken.
- Flipflop outputs cannot change even if the outputs of the combinational circuit driving their inputs change in value.
- Thus, transition from one state to the next occurs only at predetermined intervals dictated by the clock pulses.




(a) Block diagram

 

(b) Timing diagram of clock pulses
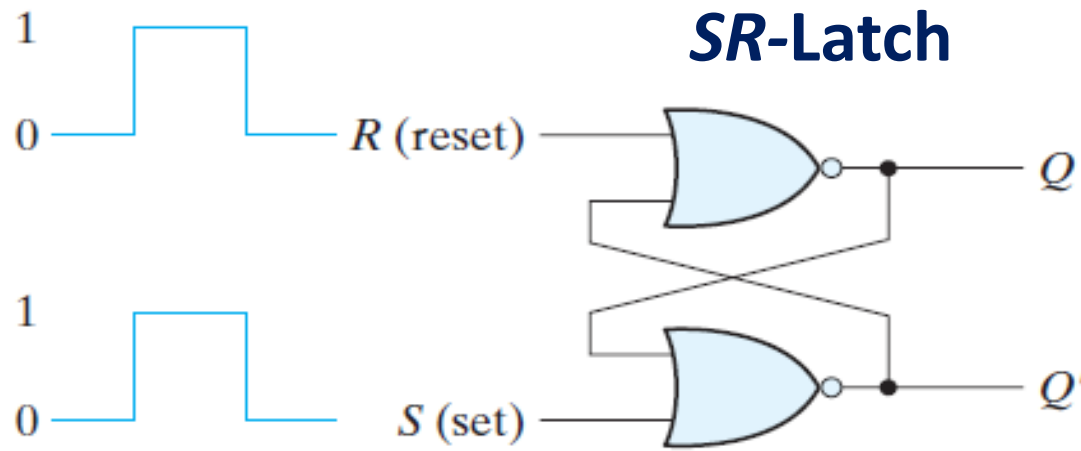
## STORAGE ELEMENTS: LATCHES

- A storage element in a digital circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states.
- Major differences among various types of storage elements are in the number of inputs they possess and in the manner in which the inputs affect the binary state.
- *Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches ; those controlled by a clock transition are flip-flops.*
- Latches are level sensitive devices; flip-flops are edge-sensitive devices.
- Latches are basic circuits from which all flip-flops are constructed.
- Latches are useful for storing binary information and for the design of asynchronous sequential circuits but not practical for use as storage elements in synchronous sequential circuits.



(a) Logic diagram


$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

(b) Function table

- $SR$  latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates.
- When output  $Q = 1$  and  $Q = 0$ , the latch is said to be in *set state*.
- When  $Q = 0$  and  $Q = 1$ , it is in *reset state*.
- Outputs  $Q$  and  $Q$  are normally complement of each other.
- When both inputs are equal to 1 at the same time, a condition in which both outputs are equal to 0 (rather than be mutually complementary) occurs.
- If both inputs are then switched to 0 simultaneously, device will enter an unpredictable or undefined state or a metastable state.
 
## SR-Latch


- Under normal conditions, both inputs of latch remain at 0 unless state has to be changed.
- Application of a momentary 1 to S input causes latch to go to **set** state. ( $S = 1, R = 0$ )
- S input must go back to 0 before any other changes take place, in order to avoid occurrence of an undefined next state that results from forbidden input condition.
- Two input conditions cause circuit to be in the **set** state.
- Removing active input from S leaves the circuit in the same state.
- ( $S = 1, R = 0, Q = 1, Q' = 0$ )
- It is then possible to shift to the **reset** state by momentary applying a 1 to R input.
- Removing active input from R leaves the circuit in same state.
- When both inputs S and R are equal to 0, latch can be in either set or reset state, depending on which input was most recently a 1.*



S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)
 
## SR-Latch


- If a 1 is applied to both  $S$  and  $R$  inputs of the latch, both outputs go to 0.
- This action produces an undefined next state, because the state that results from the input transitions depends on the order in which they return to 0.
- It also violates the requirement that outputs be the complement of each other.
- In normal operation, this condition is avoided by making sure that 1's are not applied to both inputs simultaneously.



$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)
 
## SR-Latch

- SR latch can also be constructed with **two cross-coupled NAND gates**.
- It operates with both inputs normally at 1, unless the state of the latch has to be changed.
- Application of 0 to S input causes output Q to go to 1, latch is in **set** state.
- When S input goes back to 1, circuit remains in the **set** state.
- After both inputs go back to 1, state of the latch can be changed by R= 0.
- This causes circuit to go to **reset** state and stay there even after both inputs return to 1.
- When both inputs equal to 0 at the same time, condition is forbidden for NAND latch.
- This input combination that should be avoided.




$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)

## SR-LATCH WITH A CONTROL INPUT

- Input signals for NAND require complement of those values used for NOR latch.
- Since NAND latch requires a 0 signal to change its state, it is referred as an  $S'R'$  latch.
- Operation of basic  $SR$  latch can be modified by providing an additional input.
- Signal that determines (controls) *when* the state of latch can be changed by determining whether  $S$  and  $R$  (or  $S'$  and  $R'$ ) can affect circuit.
- It consists of basic  $SR$  latch and two additional NAND gates.
- Control input  $E_n$  acts as an *enable* signal for other two inputs.
- **Outputs of NAND gates stay at logic-1 level as long as enable signal remains at 0.**


$E_n$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

 


 
## SR-LATCH WITH A CONTROL INPUT


- When  $E_n$  goes to 1, information from  $S$  or  $R$  input is allowed to affect latch.
- The **set** state is reached with  $S = 1$ ,  $R = 0$ , and  $E_n = 1$  (active-high enabled).
- To change to **reset** state, inputs must be  $S = 0$ ,  $R = 1$ , and  $E_n = 1$ .
- In either case, when  $E_n$  returns to 0, circuit remains in its current state.
- Control input disables circuit by applying 0 to  $E_n$ , so that the state of the output does not change regardless of the values of  $S$  and  $R$ .
- Moreover, when  $E_n = 1$  and both  $S$  and  $R$  inputs are equal to 0, the state of the circuit does not change.



$E_n$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

 
## SR-LATCH WITH A CONTROL INPUT

- An indeterminate condition occurs when all three inputs are equal to 1.
- This condition places 0's on both inputs of basic *SR* latch, which puts it in *undefined state*.
- When  $E_n$  goes back to 0, one cannot conclusively determine next state, because it depends on whether *S* or *R* input goes to 0 first.
- This indeterminate condition makes circuit difficult to manage, and it is seldom used in practice.
- Nevertheless, *SR* latch is an important circuit because other useful latches and flip-flops are constructed from it.





$E_n$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

# SR-Flip Flops

 


Clk	S	R	Q	Q'
0	X	X	Memory	
1	0	0	Memory	
1	1	0	1	0
1	0	1	0	1
1	1	1	Not used	

 
 


- Inputs are applied when clock is 0 and then enable the clock to transfer the inputs to output.

## D-Flip Flops

 

Clk	D	Q	Q'
0	X	Memory	
1	1	1	0
1	0	0	1
1	1	Not used	

  

- No need to put  $S = 0$  and  $R = 0$  for memory.